

Prelab Sheet for "Electrical Circuits"

Section _____

Your Name _____

correct 70 x 2.5 = score (max) 25

10 chances to make 90

Signatures

- (2) 1. Substances having electrons that can move readily in response to an electric field are called conductors; other substances are called insulators
2. Complete the table by giving each quantity's symbol, unit's name, and unit's symbol

Quantity	Symbol	Unit's Name	Unit's Symbol
Charge	q	coulomb	C
Current	I	amp (ampere)	A
Voltage	V	volt	V
Resistance	R	ohm	Ω
Power	P	watt	W


- (2) 3. Electric charge flows in a circuit because of a (two words) potential difference
- (4) 4. Give four synonyms for "a thing that hampers the flow of charge and extracts energy from it as it passes." resistance load device resistor

- (4) 5. Name the four factors on which a conductor's resistance depends. resistivity length cross-sectional area temperature

- (3) 6. In order for an electric current to perform a practical task, what three criteria are necessary? source of voltage closed conducting path a device to do the task
OR BATTERY OR LOAD

- (8) 7. Identify by name each part of the circuit indicated by a letter.

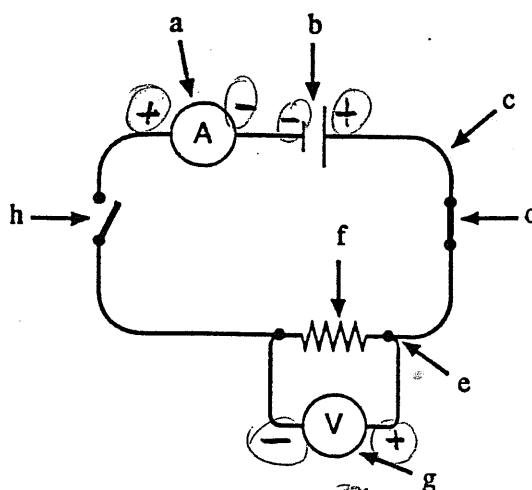- a. ammeter
- b. battery
- c. wire (conductor)
- d. closed switch
- e. junction
- f. resistance (load)
- g. voltmeter
- h. open switch



- (6) Mark + and - on the appropriate sides of a, b, and g in the circuit.

- (2) What needs to be done to obtain a current through the circuit? circuit must be closed
(switch must be closed)
- (2) The electron movement will be (clockwise, counterclockwise). The current's direction will be (clockwise, counterclockwise).

THESE CAN SUB. FOR FIRST 3 PROBLEMS

8. A 6 V battery is wired to a resistor, and an ammeter gives a reading of 0.3 A in the circuit. What is the resistor's resistance? Show setup.
- Setup: $R = \frac{V}{I} = \frac{6V}{0.3A} = 20\Omega$ Answer: 20Ω
9. How much power is used by the resistor of Question 8? Show setup.

Setup: $P = IV = (0.3A)(6V) = 1.8W$ Answer: 1.8W

10. A voltmeter is always connected in (series, parallel); an ammeter in (series, parallel).
A (black, red) wire attaches to the + terminal of a battery; a (black, red) one to the negative.


11. As the current in a wire gets greater, the wire gets hotter

12. For each circuit, calculate the current in the circuit and through each resistance. Show setup and answer in each case. (Hint: In c and d find R_T by use of Equation 4 or Equation 5.)

WE DID #12 IN CLASS, SO MOST SHOULD BE CORRECT

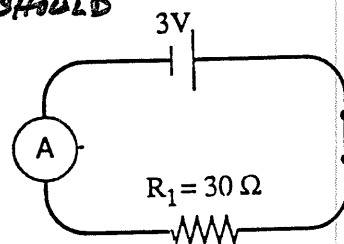
- a. Setup: I in circuit 0.1A

$I = \frac{V}{R} = \frac{3V}{30\Omega} = 0.1A$ I in R_1 0.1A



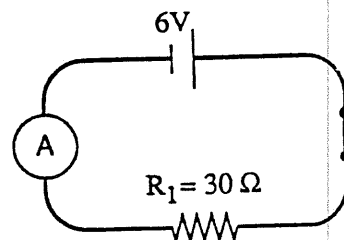
- b. Setup: I in circuit 0.2A

$I = \frac{6V}{30\Omega} = 0.2A$ I in R_1 0.2A



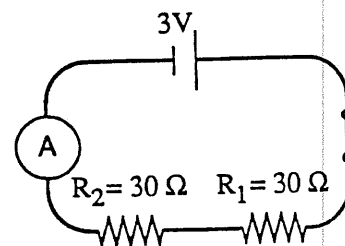- c. Setup: I in circuit 0.05A

$R_T = 30\Omega + 30\Omega = 60\Omega$ I in R_1 0.05A
 $I = \frac{V}{R} = \frac{3V}{60\Omega} = 0.05A$ I in R_2 0.05A




- d. Setup: $I_T = \frac{3V}{15\Omega} = 0.2A$ I in circuit 0.2A

$R_T = \frac{(30\Omega)(30\Omega)}{30\Omega + 30\Omega} = \frac{900\Omega^2}{60\Omega} = 15\Omega$ I in R_1 0.1A

$\frac{1}{R_T} = \frac{1}{30\Omega} + \frac{1}{30\Omega} = \frac{2}{30\Omega} = \frac{1}{15\Omega}$ I in R_2 0.1A
 $I_T = I_1 + I_2$

$R_T = \frac{15\Omega}{1} = 15\Omega$

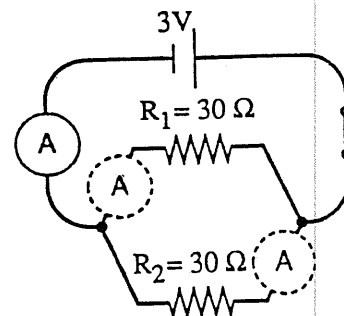

Data Sheet for "Electrical Circuits"

Section (1) Partner's Last Name _____ Your Name _____

Part A: A Simple Circuit

1. Set up the circuit shown in Figure 11-A, using the 3V battery, the first bulb of the three-bulb board, and 2 wires. On Figure 11-A, draw *red* arrows showing the direction of the *current* when the switch is on. Draw *black* arrows showing the direction of *electron flow*. Turn on the switch. What is observed? BULB LIGHTS (1)
With the switch still on, loosen the bulb. What is observed? LIGHT GOES OUT (1)
Why? CIRCUIT IS BROKEN (2)

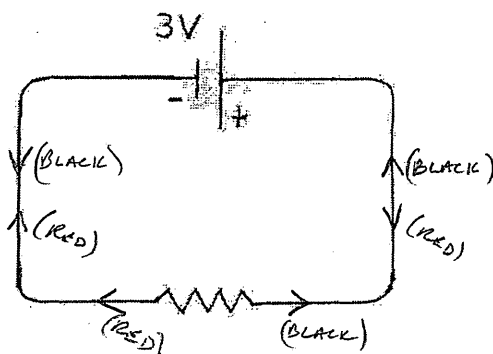


Figure 11-A

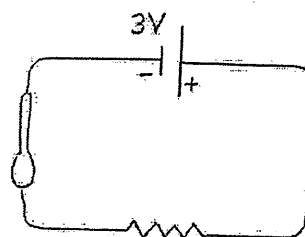



Figure 11-B

2. Tighten the bulb (not too tight). Turn off the switch. Use another wire to set up the circuit shown in Figure 11-B, where a metal spoon is made part of the circuit. Turn on the switch. What is observed? BULB LIGHTS (1)
Is the metal spoon a conductor, or an insulator? CONDUCTOR (1)

Turn off the switch and replace the metal spoon with the plastic spoon.

- Turn on the switch. What is observed? NOTHING / BULB DOES NOT LIGHT (1)
Is the plastic spoon a conductor, or an insulator? INSULATOR (1)

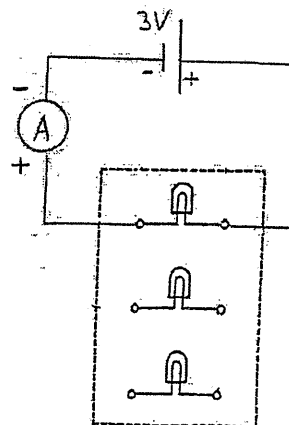3. Turn off the switch, remove the plastic spoon, and connect the ammeter in its place as shown in the figure to the right.




Turn on the switch and measure and record the current to the nearest 0.01 A. .19 A
 Turn off the switch. Disconnect the ammeter, and replace it with one wire, as previously. Connect the ammeter between the positive terminal of the battery and the bulb. Check to see that the positive connection on the ammeter is toward the positive side of the battery. Turn on the switch and measure and record the current to the nearest 0.01 A. .19 A
 Was the current the same (within experimental error) on both sides of the circuit? YES

(2 A, V)

(2)

(1)

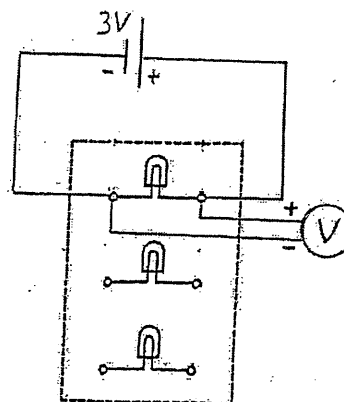4. Turn off the switch, disconnect the ammeter, and again use one wire to connect the positive terminal of the battery to the bulb. Connect a wire to the common input of the voltmeter and a wire to its middle input, where the scale will read 0 to 3 V.



Turn on the switch. Touch the voltmeter's red connection (+) to the positive side of the bulb and the black connection (-) to the negative side of the bulb as shown in the figure above. This measures the voltage across the bulb. Read the voltage, to the nearest 0.05V, on the scale that goes from 0 to 3V. 3.00V

(3) 1 VALUE
1 3 S.F.
1 UNITS

In similar fashion, being careful to touch the correct leads to the proper places, measure the voltage across the battery and then turn off the switch. 3.00V

(2)

Use the value of the current from Part A.3 and of the voltage across the bulb, along with Ohm's law, to calculate the resistance of the bulb.

Setup: $R = \frac{V}{I} = \frac{(3.00V)}{.19A}$

Answer: 15 Ω

(5) 2 SET UP
1 A
1 2 S.F.
1 U

Use $P = IV$ to find the power used by the bulb.

Setup: $P = IV = (.19A)(3.00V)$


Answer: .57 W

(4) 2 SET UP
1 A
1 U

Part B: The Effect on Current of Changes in Voltage and Resistance

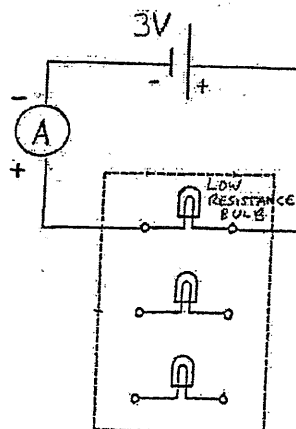1. Use the same setup as in A.3, with the **ammeter** in the circuit. Turn on the switch and note the brightness of the bulb.

Turn off the switch and replace the regular bulb with one that has lower resistance as shown in the figure on the right.



Before turning on the switch, use Ohm's law ($I = V/R$) to predict what will happen to the current (I) in the circuit when the battery voltage (V) stays the same, and the bulb resistance (R) is decreased. LARGER (larger/smaller/same) (ACCEPT ANY ANSWER) (1)

An increase in current will cause a brighter bulb; a decrease in current will cause a dimmer bulb. According to your prediction of the change in current, should this bulb be brighter, or dimmer, than the first bulb? BRIGHTER (ACCEPT ANY ANSWER) (1)

Now, turn on the switch. Results? Current value: .42 A Brightness: BRIGHTER
Were the changes in current and brightness of the bulb consistent with Ohm's law? YES (yes/no) (4)


Turn off the switch and replace the low resistance bulb with the original bulb.

2. Change the voltage from 3V to 6V. Keep the ammeter connected as shown in the figure below. According to Ohm's law, if the resistance stays the same and the voltage increases, what should happen to the current?

LARGER (ACCEPT ANY ANSWER)
(larger/smaller/same)

Therefore, what should happen to the brightness of the bulb?

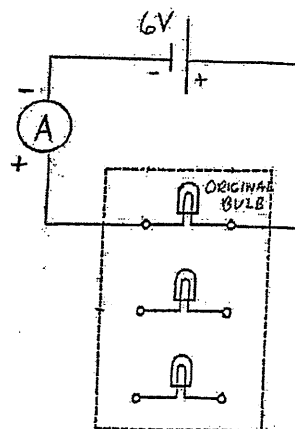BRIGHTER (ACCEPT ANY ANSWER)
(brighter/dimmer/same)



Turn on the switch. What is the value for the current? .27 A
Is the bulb brighter or dimmer, with the 6 V than with the 3 V source? BRIGHTER (2)

Carefully use the **voltmeter** to measure the voltage across the bulb. Be sure the black connection on the voltmeter is connected to the side of the bulb connected to the negative side of the battery. Voltage: 5.8V (2)

Turn off the switch. Use Ohm's law to find the bulb's resistance when this voltage is used.

Setup: $R = \frac{V}{I} = \frac{5.8V}{.27A}$

Answer: 21 Ω (4)

Is the bulb's resistance still the same as found in Part A.4 where 3 V were used?

NO (yes/no). Ohmic resistors have constant resistance for any current. (1)

Therefore, is a light bulb an *ohmic*, or a non-*ohmic*, resistance? NON-OHMIC (1)

Use $P = IV$ to find the power now used by the bulb.



Setup: $P = IV = (.27A)(5.8V)$

Answer: 1.57 W (4)

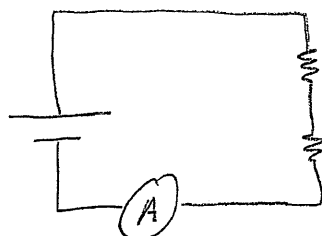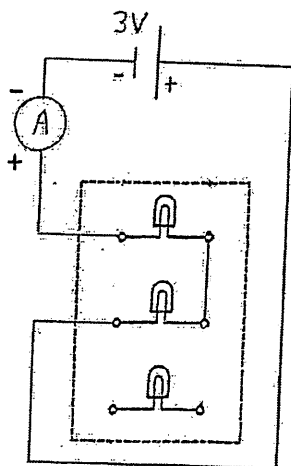Part C: A Series Circuit

Note: Be sure to switch the voltage back to 3 V!

- Set up the bulb board, the 3 V battery, and the ammeter so that two regular bulbs are connected in series as shown in the figure below. In the space at the right, sketch a schematic of the circuit using the shorthand notation shown on page 129 of the lab manual.



(5)

Get the instructor's approval (initials) here *before turning on the switch.*

[Handwritten initials]

(1)

Turn on the switch. Are the bulbs equally bright? YES

(1)

Are they brighter, or dimmer, than when only one regular bulb was in the circuit?

DIMMER

(1)

What does the brightness indicate about the current through each bulb?

LESS

(1)

What is the value given by the ammeter for the current through the two bulbs in series? .14 A

(2)

Is the current less than in Part A.3, where only one bulb was used? YES

(1)

- Turn off the switch. Connect all **three** bulbs in series.

Before turning on the switch, predict if all the bulbs will be of equal brightness.

YES (yes/no)

(1)

Will they be brighter, dimmer, or the same as when two bulbs were in the circuit?

DIMMER

(1)

Now, turn on the switch and test your brightness predictions. Results? DIMMER

(1)

What does this indicate about the current through the bulbs? LESS

(1)

What is the value given by the ammeter for the current for three bulbs in series?

.12 A

(2)

Is that less than the current when only two bulbs were in series? YES

(1)

With the switch still on, loosen one of the bulbs. What happens, and why?



ALL GO OUT - THE CIRCUIT IS BROKEN / OPEN

(2)

Retighten the bulb and turn off the switch.

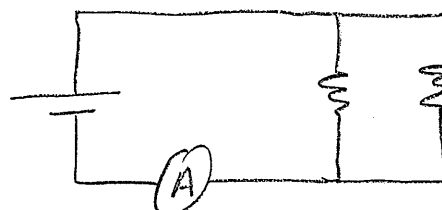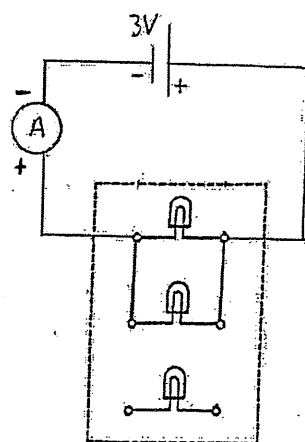Part D: A Parallel Circuit

- Set up the bulb board, the 3V battery, and the ammeter, so that two bulbs are connected in **parallel** as shown in the figure below. In the space at the right, sketch a schematic of the circuit using the shorthand notation shown on page 129.



Get the instructor's approval (**initials**) here *before turning on the switch.* LD

According to the reading assignment in the lab manual, should the current through each of the two bulbs be greater, or less, than when the two were in series? GREATER

Turn on the switch. Are the bulbs equally bright? YES

Are the bulbs brighter, or dimmer, than when the two bulbs were in series? BRIGHTER

What does the brightness indicate about the current through each bulb? LARGER / GREATER

What is the value for the total current, as given by the ammeter? .35 A

Is this less, more, or the same as when two bulbs were in series (see Part C.1)? MORE


Is this less, more, or the same as when only one bulb was used (see Part A.3)? MORE

Do two bulbs in parallel really allow more current than just one bulb by itself? YES

Turn off the switch.


Connect the ammeter to measure the current through one bulb as shown in the figure below. Turn on the switch and measure the current then turn off the switch.

What is the current? .18 A

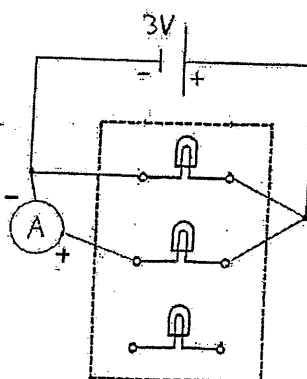

Connect the ammeter to measure the current through the other bulb as shown in the figure below. Repeat the current measurement. What is the current? .19 A

2

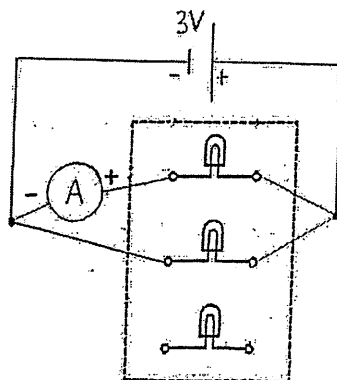

Do the last two current values add up to the total current (allowing for experimental error)? YES

(1)

2. Turn off the switch. Connect all three bulbs in parallel. *Before turning on the switch*, predict whether all the bulbs will be of equal brightness. Will they be brighter, or dimmer, than when only two bulbs were in the circuit? SAME (ACCEPT ANY ANSWER)

Turn on the switch and test your brightness predictions. Results? SAME OR EQUAL (1)

What does this indicate about the current through the bulbs? SAME OR EQUAL (1)

What is the value for the current, as given by the ammeter? .53 A (2)

With the switch still on, loosen one of the bulbs. What happens, and why?

THE OTHER TWO ARE NOT AFFECTED (1)

Turn off the switch, and then disconnect all wires and meters.